

**Bihar Engineering University, Patna**  
**Special Examination – 2023**

**Course: B.Tech.**  
**Code: 100403**

**Subject: Digital Electronics**

**Time: 03 Hours**  
**Full Marks: 70**

**Instructions:-**

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

**Q.1 Answer any seven question only:**

**[2 x 7 = 14]**

- (a) Define Dynamic RAM.
- (b) The resolution of a 10-bit AD converter for an input range of 10 V is approximately\_\_\_\_\_.
- (c) The parameter through which 16 distinct values can be represented is known as \_\_\_\_\_.
- (d) Define Multiplexing.
- (e) Write the significance of Truth table.
- (f) Write the differences between Combinational and Sequential circuit.
- (g) A hexadecimal odometer displays F52F. The next reading will be \_\_\_\_\_.
- (h) The basic property of Sequential circuit is \_\_\_\_\_.
- (i) How many entries will be in the truth table of a 4-input NAND gate?
- (j) What is Dual Slope ADC?

**Q.2** What are weighted, non-weighted, cyclic and self-complementary codes? Explain each with examples. **[14]**

**Q.3** Design a BCD to 7-segment display decoder circuit using logic gates. **[14]**

**Q.4** Design a 3-bit parallel comparator A/D convertor that provides output in 2's complement format. **[14]**

**Q.5** Design full adder using the following: **[14]**

- (i) 8:1 mux
- (ii) 4:1 mux

**Q.6** What is binary shift register? Write down their application. **[14]**

**Q.7** Minimize the following expression using k-map **[14]**  
 $f(P, Q, R, S) = \sum m(0, 1, 4, 5, 7, 12, 13)$

**Q.8** Describe the procedure to design Mod-6 counter. **[14]**

**Q.9** Write short notes on any two of the following **[7x2=14]**

- (i) RAM (ii) ROM (iii) CMOS logic
- (iv) Operation of TTL logic circuit working as NAND Gate

**Bihar Engineering University, Patna**  
**End Semester Examination -2023**

**Course: B.Tech**  
**Code: 100403**

**Semester: IV**  
**Subject: Digital Electronics**

**Time: 03 Hours**  
**Full Marks: 70**

**Instructions:-**

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. **1** is compulsory.

**Q.1 Answer any seven Question only:**

**[2 x 7 = 14]**

- (a) Convert the Decimal number (108.025) to their binary equivalent.
- (b) Draw Truth table of JK flip flop.
- (c) Draw the truth table and logic circuit of Half-adder.
- (d) Write the difference between combinational & Sequential circuit.
- (e) Draw timing diagram of SR flip-flop.
- (f) Find 2's complement of 1011011.
- (g) Number of 2:1 mux requires designing 256:1 mux is .....
- (h) Add hexadecimal number 2ABC & 98F2.
- (i) Discuss Universal gates.
- (j) What is the use of K-map?

**Q.2** Implement the following function using only NAND gate  
 $F(A,B,C)=\sum m(0,1,2,3,7)$ .

**[14]**

- Q.3** (a) Realize XNOR logic function using NAND gate only. [7]  
(b) Simplify  $Y = ABC + AB\bar{C} + A\bar{B}C$  [7]

**Q.4** A logic circuit has four inputs A,B,C,D and output Y. Y=1 when A & B are both 1, subjected to the condition that C and D are both low or both high. Design the logic circuit.

**[14]**

**Q.5** Explain Master-slave flip flop. What are race around condition?. How it can be circumvented with the help of Master-slave flip flop.

**[14]**

- Q.6** (a) Design 8 to 3 line Encoder circuit. [7]  
(b) Implement NAND gate using TTL logic family. [7]

**Q.7** Summarize the design procedure for a synchronous sequential circuit.

**[14]**

- Q.8** (a) Explain the working of R-2R Ladder DAC. [7]  
(b) Design 3-bit binary counter using T flip-flop. [7]

**Q.9** Write short notes on the following:

**[7\*2=14]**

- (a) Binary Parallel Adder
- (b) Digital IC logic families



**B.Tech 4th Semester Exam., 2022**

( New Course )

**DIGITAL ELECTRONICS**

*Time : 3 hours*

*Full Marks : 70*

*Instructions :*

- (i) The marks are indicated in the right-hand margin.*
- (ii) There are **NINE** questions in this paper.*
- (iii) Attempt **FIVE** questions in all.*
- (iv) Question No. **1** is compulsory.*

**1.** Answer any seven of the following :  $2 \times 7 = 14$

- (a) What is the next number in the following octal counting sequence?

724, 725, 726, 727, \_\_\_\_\_

- (b) What do you mean by a positive logic system and a negative logic system?

- (c) Subtract using 9's complement :

745.81 - 436.62

( 2 )

- (d) The following operation is correct for at least one number system. Find the correct number system :

$$1234 + 5432 = 6666$$

- (e) What is a tri-state logic?
- (f) Which are the fastest logic family and the slowest logic family?
- (g) Which memory technology needs the least power?
- (h) What is a register? What is a shift register?
- (i) What is a master-slave flip-flop?
- (j) Fill in the blank :

$$(100101000111)_{(BCD)} = ( \text{ \_\_\_\_\_\_ } )_{10}$$

2. (a) Which of the following are analog quantities and which are digital?

Number of atoms in a sample of material, Altitude of an aircraft, Pressure in a bicycle tire, Current through a speaker, and Timer setting on a microwave oven.

( 3 )

(b) What do you mean by self-complementing code? Write two self-complementing codes.

(c) If the waveforms A and B shown in Fig. 1 are applied to a two-input XOR gate, determine the output waveform :

 


Fig. 1

4+4+6

3. (a) Perform the following in excess-3 code using the 10's complement method :

$$239 - 597$$

(b) Design and implement a 4-bit binary to Gray converter.

(c) Reduce the following expression using K-map and implement it in AOI logic as well as in NOR logic :

$$F = \Pi M(0, 1, 2, 3, 4, 7) \quad 5+4+5$$

( 4 )

4. (a) Reduce the following expression and implement it using universal logic gate :

$$\Sigma m(1, 5, 6, 12, 13, 14) + d(2, 4)$$

- (b) Use a multiplexer to implement the logic function  $F = A \oplus B \oplus C$ . 7+7

5. (a) Determine the Q-output waveform if the inputs shown in Fig. 2 are applied to the gated D-latch which is initially RESET :

 


Fig. 2

- (b) Design the conversion circuit for S-R flip-flop to J-K flip-flop. 7+7

6. (a) What is basic difference between a counter and a shift register?
- (b) With neat diagrams, explain the working of the following types of shift registers :
- (i) Serial-in, serial-out
  - (ii) Serial-in, parallel-out
- (c) Design and implement a mod-10 asynchronous counter using *T* flip-flops.  
3+6+5
7. (a) Design and implement a synchronous 3-bit up/down counter using *J-K* flip-flops.
- (b) Determine the resolution of—
- (i) 6-bit DAC;
  - (ii) 12-bit DAC
- in terms of percentage.
- (c) What is the resolution of a 9-bit DAC which uses a ladder network? What is this resolution expressed as a percentage? If the full-scale output voltage of this converter is +5 V, what is resolution in volts?  
5+4+5

8. (a) For the 4-bit weighted resistor DAC shown in Fig. 3, determine the—

(i) weight of each input bit if the inputs are 0 V and 5 V;

(ii) full-scale output if  $R_f = R = 1 \text{ k}\Omega$ .

Also, find the full-scale output if  $R_f$  is changed to  $500 \Omega$  :

 


Fig. 3

(b) What is a PLD? What do 'x' and 'dot' represent on a PLD diagram?

9+5

9. (a) What are the different technologies used for the fabrication of ROM memories? Determine how many  $16\text{K} \times 4$  memory circuits would be required to construct each of the following memories :

(i)  $256\text{K} \times 8$

(ii)  $128\text{K} \times 16$



( 7 )

- (b) Define Memory cell, Address and Byte.
- (c) Using the simplified connection format of a PLA, show how an  $8 \times 1$  PROM should be programmed to implement the logic function

$$F = \Sigma m(1, 4, 5, 7) \quad 4\frac{1}{2} + 4\frac{1}{2} + 5$$

★ ★ ★



**Bihar Engineering University, Patna**  
**B.Tech 4<sup>th</sup> Semester Examination, 2024**

Course: B.Tech  
Code: 100403

Subject: Digital Electronics

Time: 03 Hours  
Full Marks: 70

**Instructions: -**

- (i) The marks are indicated in the right-hand margin.
- (ii) There are **NINE** questions in this paper.
- (iii) Attempt **FIVE** questions in all.
- (iv) Question No. 1 is compulsory.

**Q.1 Answer of the following questions (any seven only):-**

[2 x 7 = 14]

- (a) What is the use of K-map?
- (b) Discuss Universal gates.
- (c) Add hexadecimal number 2ABC & 98F2.
- (d) Number of 2:1 mux requires designing 256:1 mux is .....
- (e) Find 2's complement of 1011011.
- (f) What is the function of a sample-and-hold circuit?
- (g) Define term propagation delay.
- (h) Define race around condition in JK flip flop.
- (i) What is the purpose of expanding memory size?
- (j) Differentiate between ROM and RAM.

**Q.2** (a) Realize XNOR logic function using NAND gate only.  
(b) Simplify  $Y = ABC + ABC + A\bar{B}C$

[7]  
[7]

**Q.3** A logic circuit has four inputs A,B,C,D and output Y. Y=1 when A & B are both 1, subjected to the condition that C and D are both low or both high. Design the logic circuit.

[14]

**Q.4** (a) Design 8 to 3 line Encoder circuit.  
(b) Implement NAND gate using TTL logic family.

[7]  
[7]

**Q.5** (a) Design a parallel-to-serial converter using shift registers and explain its operation.  
(b) Compare the characteristics and applications of JK and T flip-flops.

[7]  
[7]

**Q.6** (a) Explain the working principle of an R-2R ladder DAC with a detailed diagram.  
(b) Design a 3-bit flash ADC and explain its working with an example.

[7]  
[7]

**Q.7** (a) Find the Simplified logical expression for Y.  
 $Y(A, B, C, D, E) = \sum m(0, 2, 4, 7, 8, 10, 12, 16, 18, 20, 23, 24, 25, 26, 27, 28)$   
(b) Summarize the design procedure for a synchronous sequential circuit.

[7]  
[7]

**Q.8** (a) Implement S-R, T, D flip-flops using J-K flip-flop. Also show the implementation with help of State Tables.  
(b) Discuss the organization and operation of content-addressable memory (CAM).

[7]  
[7]

**Q.9** Write short notes on the following:  
(a) Binary Parallel Adder  
(b) Digital IC logic families

[7x2=14]